

Hack The Web – Minecraft III


It's so dark here—could you turn on the light?

Hehe, I have a little surprise: this redstone lamp has seven switches, and there is only one combination that makes the lamp light up. That should keep you busy for a while. I'll be back once you've found the right combination.

In this challenge, we're asked flip switches to make a Minecraft redstone lamp light up

Hack The Web – Minecraft III

Web Research

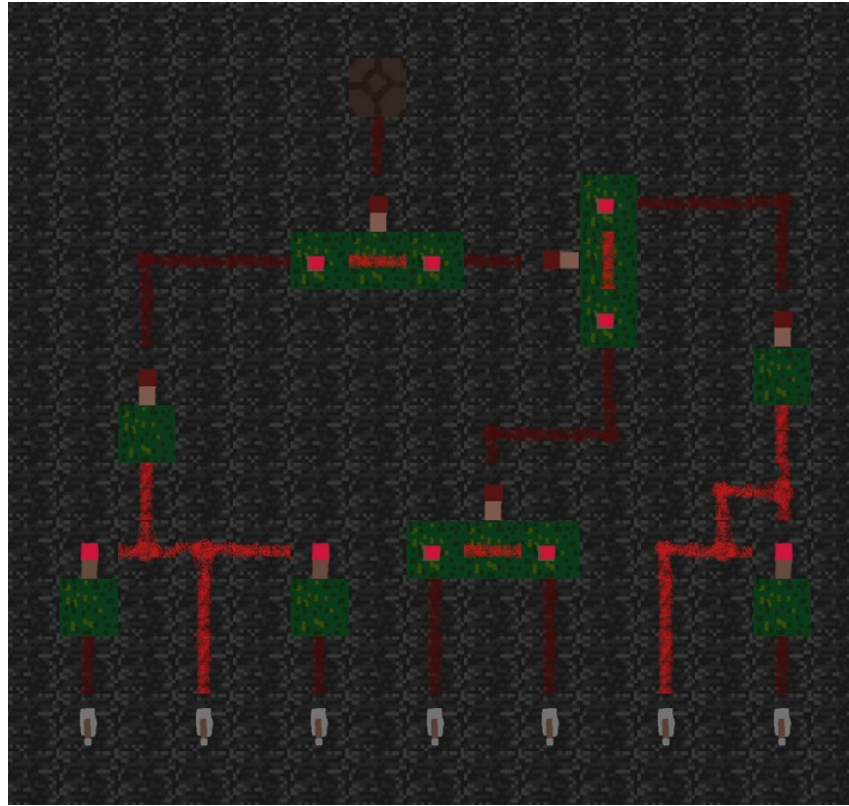

In this challenge, we're asked flip switches to make a Minecraft redstone lamp light up

Hack The Web – Minecraft III

Web Research

A redstone torch is on when the adjacent block is not powered. As soon as the block is powered, the torch turns off.


With three torches and some blocks you can build an AND gate. The middle torch only lights up when both inputs are on.

With this knowledge, you can trace the circuit back step by step and figure out the correct switch combination.

If we click on the Redstone mini guide tab, we learn that the switches at the bottom of the screen can be used as an AND gate

Hack The Web – Minecraft III


Web Research

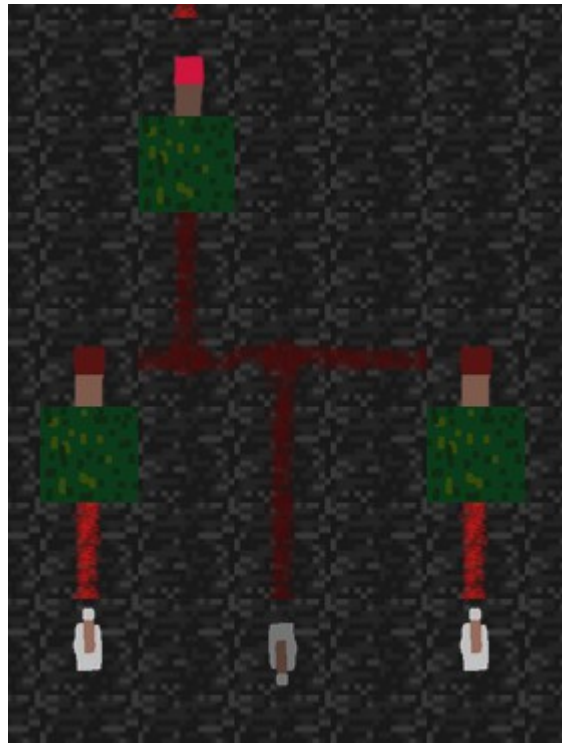

If we flip the two switches in the AND gate, it activates the torch at the next layer up

Hack The Web – Minecraft III

Web Research

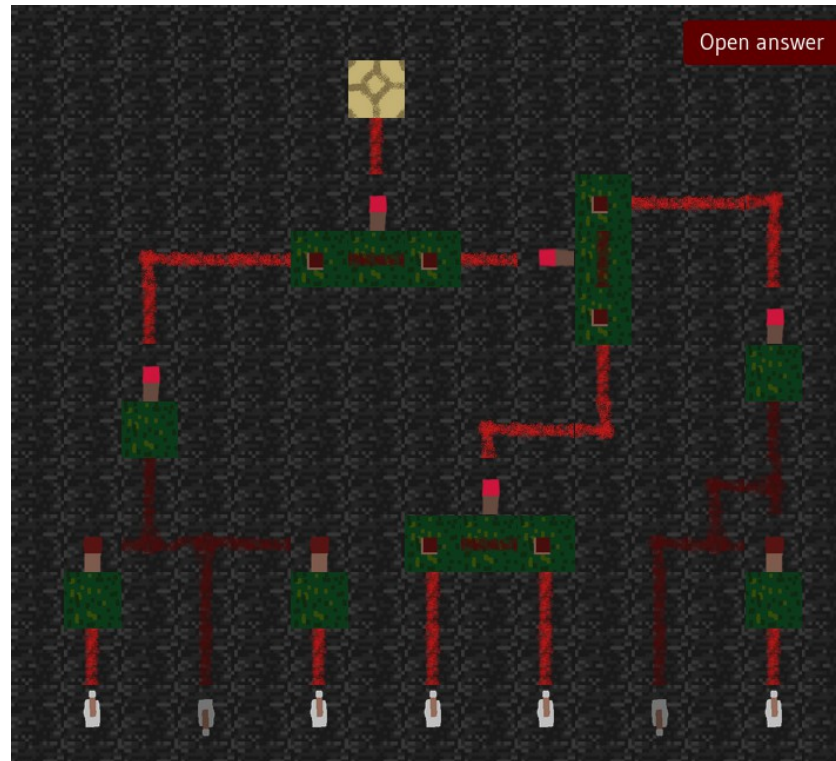

Once we've activated all of the AND gates, the redstone lamp lights up and we can obtain the answer